

---

## REQUIREMENTS NOT MET

---

- All Requirements were met.

---

## PROBLEMS ENCOUNTERED

---

- No problems were encountered.

---

## INTRODUCTION

---

We explore the characteristics of diodes, how voltage differences affect current flow and how to use diodes to create a half wave rectifier. We also explore the use of comparators and how to use them to create a circuit that can detect when a voltage is above or below a certain threshold.

---

## DISCUSSION

---

### 8.5 Pre-Lab Requirements:

#### 8.5.1 LTspice Simulations:

1. Set the input to a 1 kHz, 5 V amplitude sine wave and run a transient simulation with a stop time of 1m (.tran 1m) and plot the input and output. To use the 1N4148 diode model, right click on the diode after placing it, Pick New Diode, and then choose the 1N4148 model (Mfg. OnSemi). Save an image of the circuit and the plot of the input and output voltage for submission to canvas.

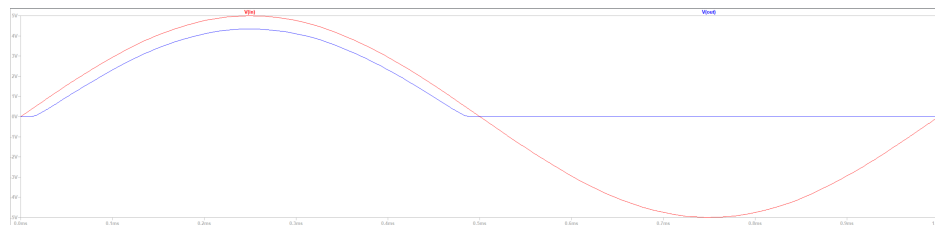


Figure 1: HALF WAVE RECTIFIER PLOT

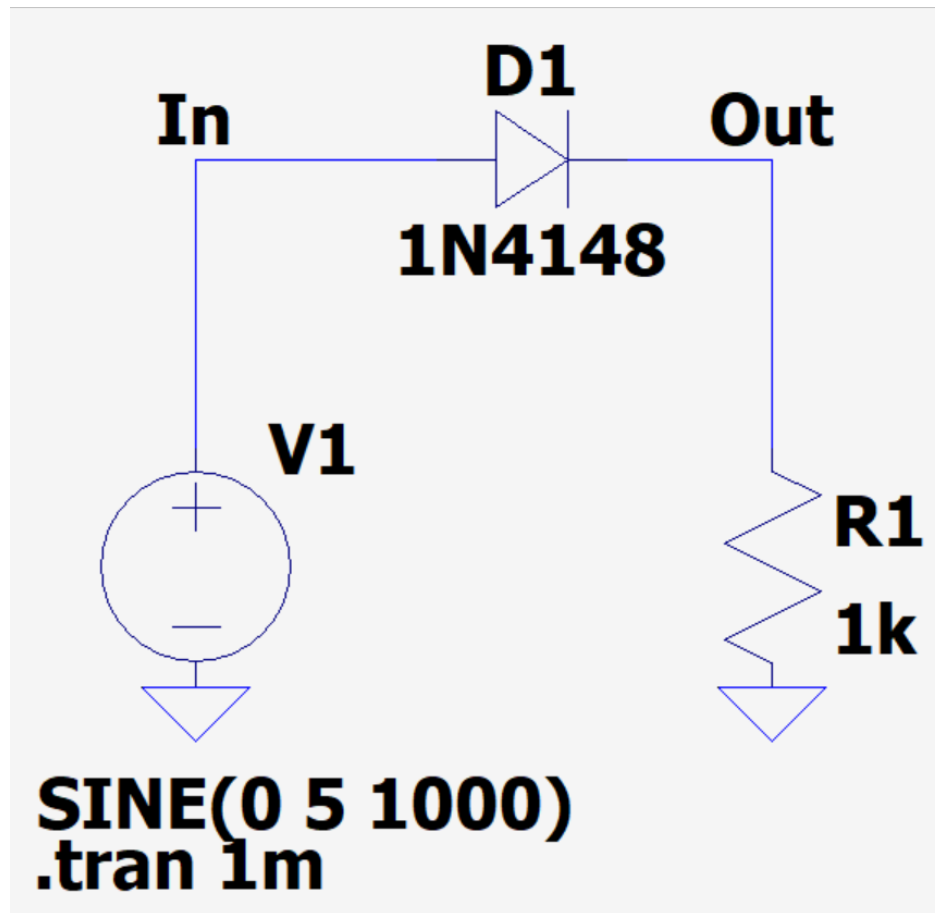


Figure 2: HALF WAVE RECTIFIER CIRCUIT

- Build the circuit in Figure 8.3 (a). Set the input to a 100 kHz, 5 V amplitude sine wave and run a transient simulation with a stop time of 50u (.tran 50u) and step through possible capacitor values using the following spice directive:

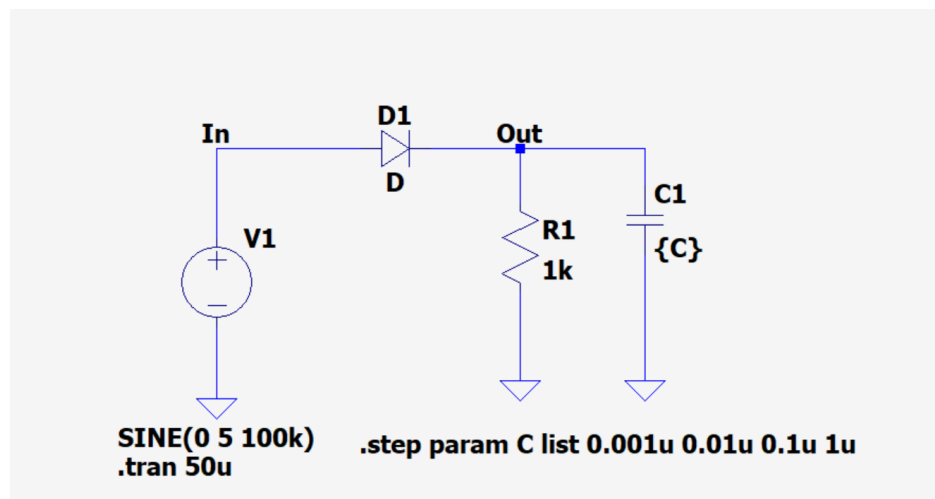


Figure 3: HALF WAVE RECTIFIER CIRCUIT WITH CAPACITOR

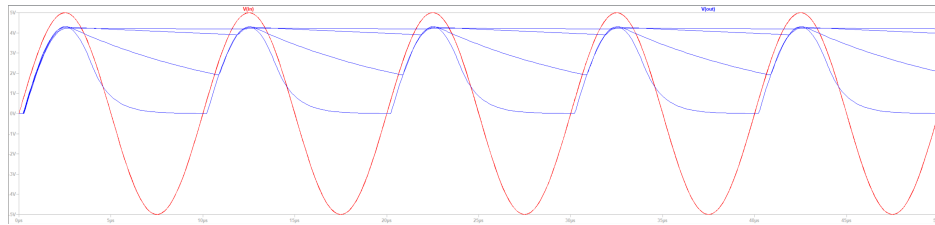


Figure 4: HALF WAVE RECTIFIER CIRCUIT WITH CAPACITOR PLOT

- Build the circuit in Figure 8.4. Use the default LED model in LTSpice, and download "slcj016.zip" file from Canvas "Lab Related Files" folder for the LM393 comparator model. Don't use the "slcj016b.zip" for the comparator model from TI because it's a newer model that doesn't work for input higher than ( $V_{cc}-2V$ ). Power the LM393 with  $\pm 5$  V. Set the input voltage to a 1 kHz, 5 V amplitude sine wave and run a transient solution with a stop time of 2m (.tran 2m). Plot the input voltage and the current through each diode. Save an image of the circuit and the plot for submission to canvas

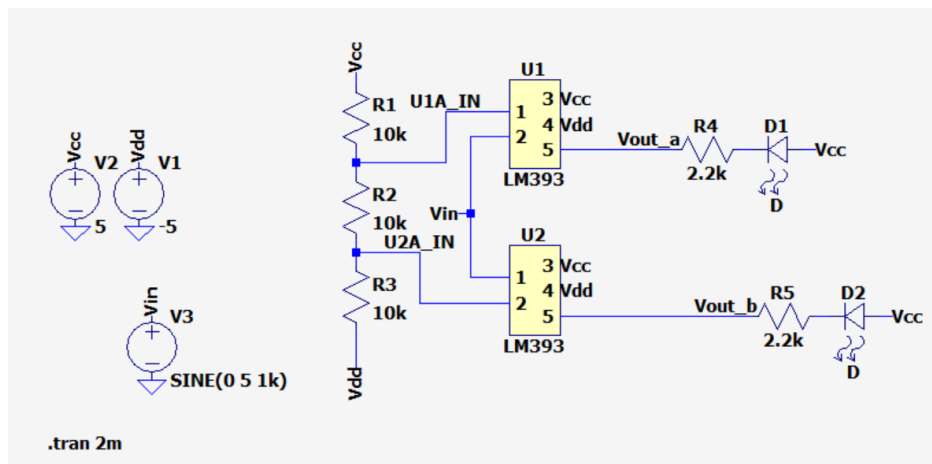


Figure 5: COMPARATOR CIRCUIT

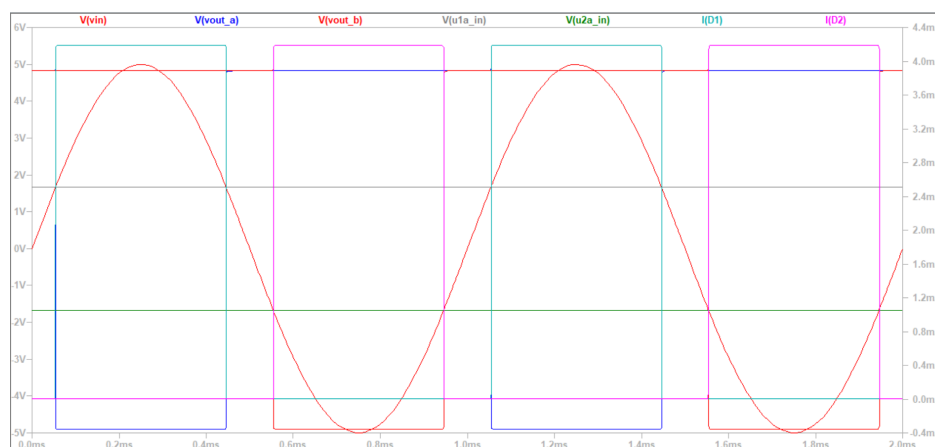


Figure 6: COMPARATOR PLOT

- Build the circuit in Figure 8.7. Power the LM393 and TLV272 with  $\pm 5$  V. Set the input voltage to a 1kHz, 0.1 V amplitude sine wave and run a transient solution with a stop time of 2m. Choose

the value for R1, 10k pot, so that the diodes conduct current and illuminate. Plot the input voltage, output of the op amp, positive and negative inputs to the comparator, and the current through both LEDs. (6 items total). Save an image of the circuit and the plot for submission to canvas.

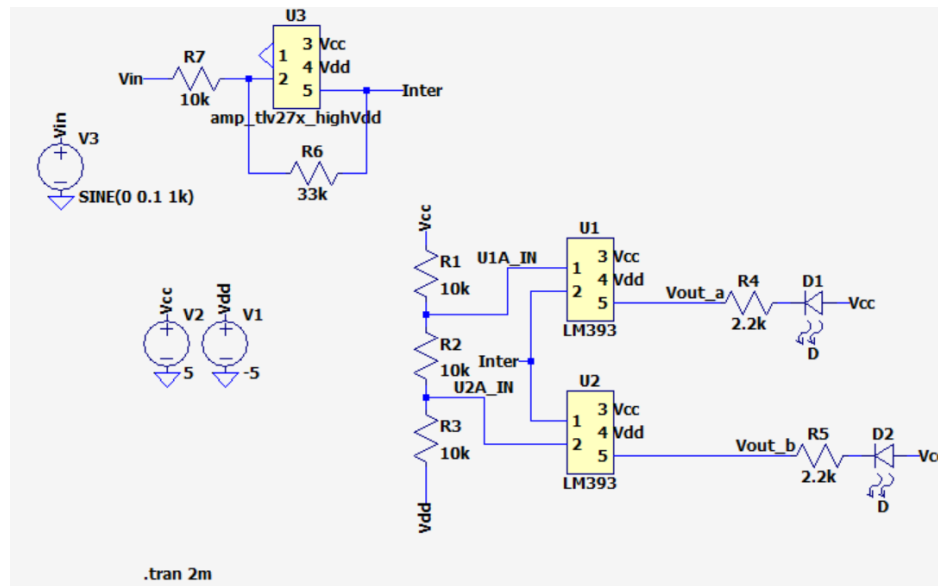


Figure 7: COMPARATOR CIRCUIT WITH OP-AMP

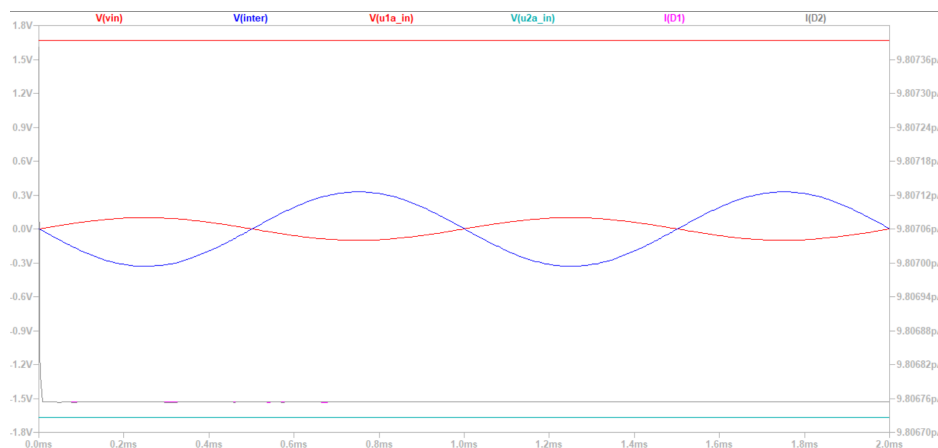


Figure 8: COMPARATOR PLOT WITH OP-AMP

### 8.5.2 Breadboard Implementation:

1. Build the circuit in Figure 8.4 on the breadboard. The following plot shows the o-scope output.

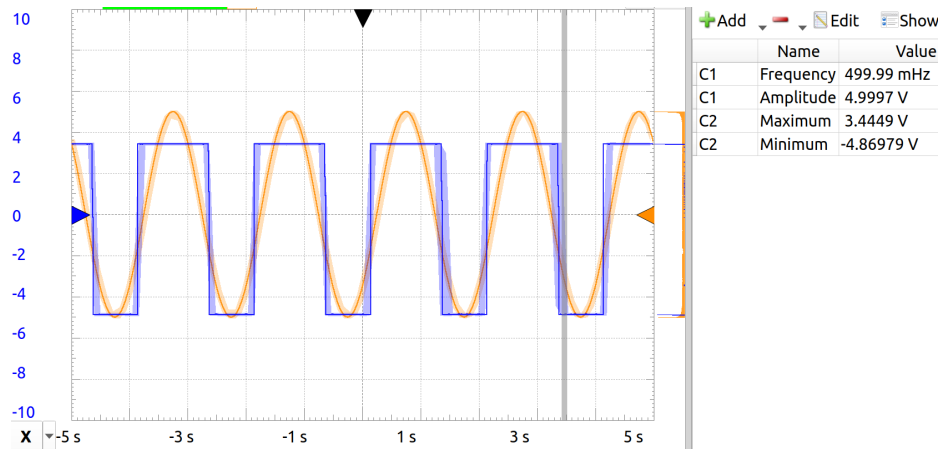


Figure 9: COMPARATOR PLOT PHYSICAL

2. Build the circuit from Section 8.5.1 - Item 1. Plot the input and output on the o-scope and save an image of the display.

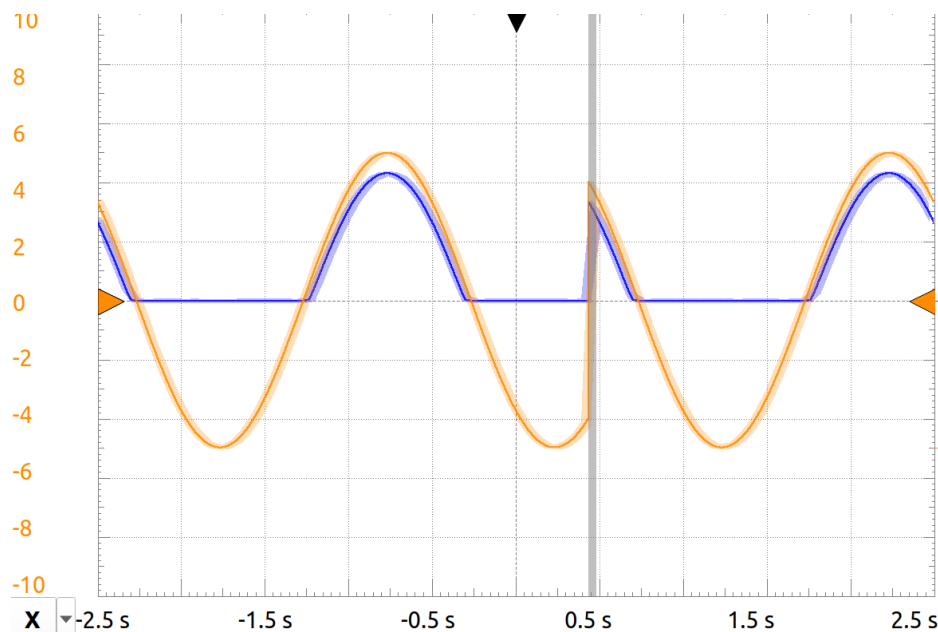


Figure 10: 8.5.1 PLOT PHYSICAL

3. Build two version of the circuit from Subsection 8.5.1 - Item 2, one with where the capacitance is 0.1  $\mu\text{F}$  and the other is 0.01  $\mu\text{F}$ . Plot the outputs of both circuits on the o-scope and save an image of the display.

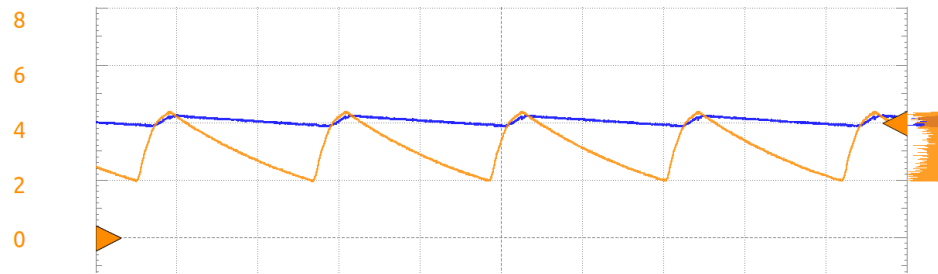


Figure 11: DIFFERENCE IN CAPS PLOT PHYSICAL

4. Build the circuit from Subsection 8.5.1 - Item 4. Set the input to a 0.5 Hz, 0.1 V amplitude sine wave. Vary the potentiometer, increase the gain, so that the LEDs illuminate when the op amp output is greater than the reference voltages. Plot the output of the gain amplifier and the output of either comparator on the o-scope and save an image of the display

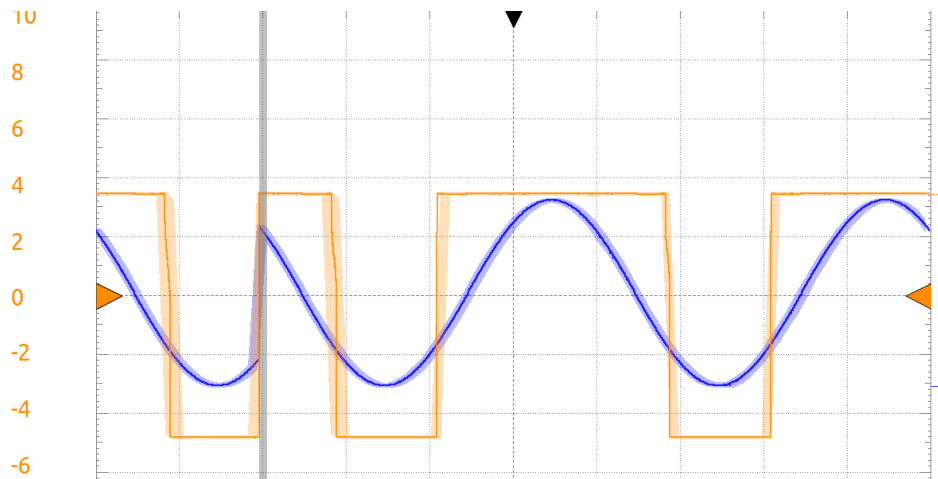


Figure 12: POTENTIOMETER PLOT PHYSICAL

---

## CONCLUSION

---

Comparatively, we first explore the first circuit brought to attention in the lab, the half-wave rectifier. A rectifier circuit is used to convert AC to DC typically with the use of diodes. The circuit can be viewed on Figure 2, The diode will only allow current to flow forwards as seen in **Figure 4**. The second circuit introduces a capacitor to the circuit. The capacitor will charge up to the peak voltage of the input signal and then discharge through the load resistor. This charging effect essentially smooths the output. In the half-wave rectifier with the capacitor, we can see the voltage level not dropping fully to zero, or dropping at a slower rate in **Figure 4**. The third circuit mentioned was the comparator circuit. The comparator circuit is used to compare two voltages and output a digital signal based on the comparison. The circuit can be viewed on **Figure 5**. The output of the comparator is either high or low depending on the voltage of the input signal. This would drive the LEDs. The fourth circuit is a comparator circuit with an op-amp. The op-amp is used to amplify the input signal. The circuit can be viewed on **Figure 7**. The output of the op-amp is then fed into the comparator circuit. The output of the comparator circuit is then used to drive the LEDs. The LEDs will light up when the voltage of the input signal is greater than the reference voltage. The reference voltage is set by the potentiometer. The potentiometer is used to adjust the reference voltage. The circuit can be viewed on **Figure 12**.